

IN THEORY, THERE IS NO DIFFERENCE BETWEEN THEORY AND PRACTICE.
BUT, IN PRACTICE, THERE IS.

YOGI BERRA

A DESIGNER KNOWS THAT HE HAS ACHIEVED PERFECTION NOT WHEN THERE
IS NOTHING LEFT TO ADD, BUT WHEN THERE IS NOTHING LEFT TO TAKE
AWAY.

ANTOINE DE SAINT-EXUPÉRY

PHYS 229

INTRODUCTION TO EXPERIMENTAL PHYSICS

ANDREW MACRAE

Introduction

Wha? and the use of the `tufte-book` and `tufte-handout` document classes.

Fundamental Quantities of Electronics

What is Electronics?

TAKE AN ELECTRONIC DEVICE which can be as simple (a flashlight) or as complicated (a smartphone) as you like. Fundamentally, these devices function by using electric and magnetic fields to push around charged particles which wiggle and bump into one another in just the right way to work as they do. All of this behaviour can be precisely calculated using Maxwell's equations (which you will see very soon in your physics career if you haven't already). Although that is what is truly what is going on "behind the scenes", it is a terribly impractical and unpleasant way of thinking about a flashlight. The goal of electronics is to encapsulate all of this complexity into much simpler abstract models. In other words, we want to simplify the flashlight into a cartoon drawing, the flashlight in the same way that we simplify the motor, suspension, and materials of a car in first year physics (figure 1.1).

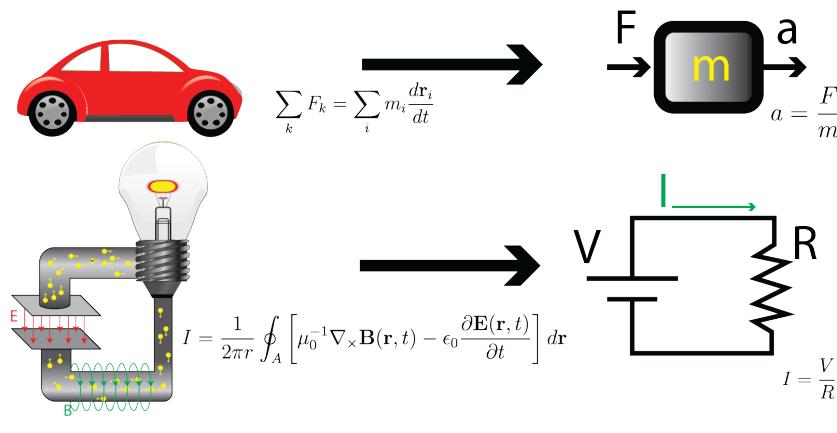


Figure 1.1: Just as you can calculate the acceleration of a car with mass m and net force F without knowing the internal details, the electronics formalism allows you calculate the current through a lightbulb given its resistance and voltage, without bothering about the particular construction or electromagnetic fields.

Fundamental Electronic Quantities: Charge, current, and Voltage

Charge

Charge is a fundamental property of a body and can be negative, positive, or zero (neutral). The S.I. units of charge is the Coulomb [C]. In nature charge is carried by (positive) protons and (negative) electrons¹ having equal magnitude but opposite sign, and the net charge of a body is entirely due to an imbalance between protons and electrons. The charge of an electron is a fundamental constant given approximately by $q_e \approx 1.602 \times 10^{-19}$ C.

¹ particle physicists will have a slightly longer list.

Current

Electronics is concerned with the transport of charge by means of electric and magnetic fields. The force on a charge q due to an electric field \mathbf{E} is given by: $\mathbf{F} = q\mathbf{E}$.² The *current* passing through an area A is defined as the amount of charge passing through this area per unit time (see fig. 1.2):

$$\text{current} = \frac{\text{net charge though surface}}{\text{unit time}} \quad (1.1)$$

The SI unit of current is the ampere which is a Coulomb per second: $1\text{A} = 1\text{C/s}$.

In electronics we deal with current sufficiently large that we can safely ignore the discrete nature of electrons and treat charge as continuous "electric fluid" that can flow (see example 1.1). This allows us to define the current more rigorously as:

$$I \equiv \frac{dq}{dt} \quad (1.2)$$

The smallest values of current in practice are on the nA (10^{-9}A) level. How many electrons pass through a wire per second for 1 nA of Current?

Solution

1 nA corresponds to $1 \times 10^{-9} \frac{\text{C}}{\text{s}}$. An electron on the other hand carries approximately $|q_e| = 1.6 \times 10^{-19}$ C of charge. A wire conducting 1 nA of current thus sees:

$$\left(1 \times 10^{-9} \frac{\text{C}}{\text{s}}\right) \times \left(\frac{1 \text{ e}}{1.6 \times 10^{-19} \text{ C}}\right) = 6.25 \times 10^9 \frac{\text{e}}{\text{s}}$$

pass through. Thus, even then, this corresponds to a flow of about 6 billion electrons per second.

² There is an additional force on a moving charge due to a magnetic field. The more general expression is given by the Lorentz force: $\mathbf{F} = q\mathbf{E} + q\mathbf{v} \times \mathbf{B}$.

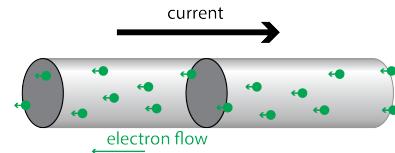


Figure 1.2: Current in a wire is the amount of charge passing a given cross section of the wire per unit time. Note that due to the negative charge of the electron, the direction of the current is opposite that of the electrons' velocity.

Note that current is defined to be in the direction of positive charge - the in a typical situation where negatively charged electrons carry the charge, the current is opposite the direction of the charges!

Typical values for current in electronic devices are on the order of millamps ($1\text{mA} = 10^{-3}\text{A}$) tens of mA is already dangerous to humans and 1A can easily start fires. We will discuss the heat generated by current shortly.

Voltage/Potential Difference

: You may recall from earlier courses that there is a quantity known as an electric potential ϕ which has units of volts, or equivalently, Newtons per Coulomb ($1\text{V} = 1\text{N/C}$). The potential due to a point charge q at distance r is given as $\phi = \frac{1}{4\pi\epsilon_0} \frac{q}{r}$ and the potential due to arbitrary charge distributions can be easily stated³. The utility of ϕ is that once given it allows you to easily determine the electrical potential energy:

³ Though not always easily calculated

$$E = q\phi \quad (1.3)$$

Being an energy, the unit of electrical potential energy is the Joule, but a convenient and commonly equivalent unit is the electron volt (eV). Self-explanatorily, this is the energy acquired by an electron when its electrical potential has changed by one volt. From the value of the electron charge and equation 1.3, we see that:

$$1\text{ eV} = 1.602 \times 10^{-19}\text{ J} \quad (1.4)$$

EXAMPLE 1.2 The Energy Scale of the LHC

Upon re-opening in 2015, the Large Hadron Collider (LHC) accelerated a beam of protons, each having an energy of nearly 6 TeV (6×10^{12} eV).

Let's Compare this to the energy of a grain of sand at a height of 1 m. The gravitational potential energy is given by $E = mgh$ Plugging in numbers, this is about 0.01 J or about 6×10^{16} eV or roughly 10000 times that of the LHC!

While this may not seem terribly efficient, recall that there are roughly 10^{24} protons in a grain of sand, so the energy *per particle* in the LHC is higher by a factor of roughly 10^{20} .

Like gravitational potential, there is no absolute scale – only differences in potential are physically meaningful. This leads us to the definition of *voltage* or, as you may now see why, *potential difference*.

Referring to figure 1.3a, the voltage between two points *A* and *B* is:

$$V = \phi(B) - \phi(A) \quad (1.5)$$

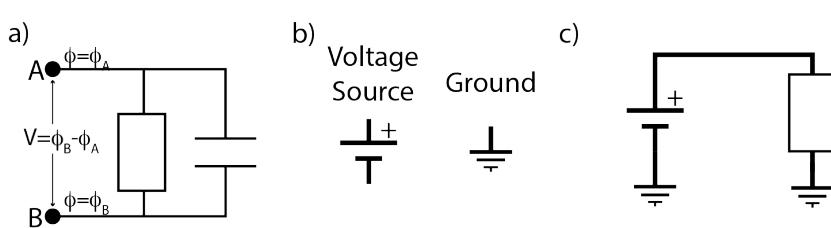


Figure 1.3: (a) The voltage between two points is defined as the difference in electric potential. (b) Circuit symbols for a voltage source and electrical ground. (c) A complete circuit connected through ground.

An ideal voltage source is something (anything) which can maintain a fixed electric potential between two points. What is meant by a non-ideal source will be discussed next lecture. Note that we don't care how it is made - it could be a battery, solar generator, or bench-top power supply. We draw an ideal voltage source, regardless of its construction as in figure 1.3b. We thus arrive at our first layer of abstraction, and will continue to replace complicated devices by little cartoon which simplify design significantly throughout the course.

A key concept is that of electrical ground, often called *ground*, or "earth". Since voltages are always defined with respect to a reference voltage, a given point in a circuit is often denoted as the 0V point, against which all other measurements are made. Ground in a circuit is so important that it is given a special symbol (figure 1.3c).

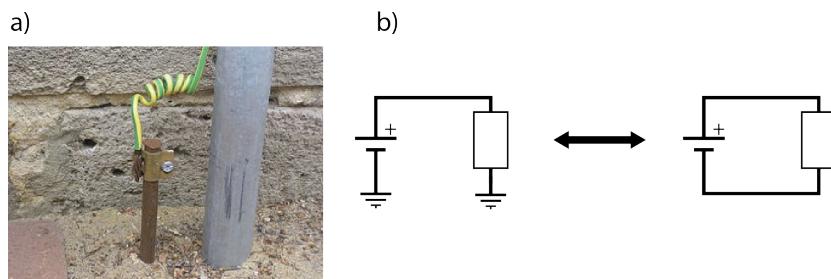


Figure 1.4: (a) A ground connection outside some house in Australia (Wikipedia CC license) (b) All ground points in a circuit are connected.

The name ground is quite literal – it is often connected to a large stake driven into the Earth (fig. 1.4a). The reason for this is that the (literal) ground provides a very large neutral body which whose potential will not change even when large amount of current are flowing into it. This would not be the case for a small metal plate which would develop a large charge imbalance and thus acquire a

positive voltage. It is important to note that although not explicitly drawn, all ground connections are connected as if by a physical wire.

The potential of the dirt outside your window need not be the reference voltage for $V = 0$. Devices powered by a battery are clearly not connected physically to earth ground. Such devices are said to be *floating* and the ground is often defined as the negative terminal of the battery. The term floating means that while the voltage **differences** are well defined along the circuit, their **absolute value** compared to an external reference are not and thus the ground level of two separate devices may float around with respect to one another. This can cause a significant danger when two floating devices are connected: since they do not have a common value for ground, they high potential differences between the two devices can exist which will damage the device.

Wires, conductors, and insulators

Just as masses in a gravitational potential will tend to accelerate to the lower potential, so to will current flow from a higher to a lower potential. To do so however, they charges need a path. As electrons are typically bound to their atoms via the coulomb force, they are typically sitting in their own potential well. This is why current isn't spontaneously flowing from one terminal of a battery to the other despite having a potential difference. Note however that if a sufficiently strong voltage is applied current will flow - even in vacuum. Certain materials however have electronic structure such that an individual electron is not bound to a particular atom and is free to move along an atomic ensemble, as long as it is replaced by another. These materials, known as conductors form the basis of electronic conductors. As long as one conductor maintains good contact with another, current may flow freely between them. The ease by which current flows is parametrized by the *conductance* ρ and has units of Siemens per meter.

At the opposite end of the spectrum are insulators which have electronic structure such that all electrons are tightly bound, giving them a very low conductivity. Insulators are as important as conductors in electronics as they provide the "walls" which keep current from flowing everywhere. It turns out that there is a third class of material we will deal with in this course which is somewhere in between a conductor and an insulator. Such a substance is known as a semiconductor. What makes semiconductors useful is that their conductivity can be easily tuned by introducing impurities and can be manipulated by injecting charges in between two different semiconductors. We will examine semiconductors in detail later in the course.

Material	Classification	Conductivity [S/m]
Copper	Conductor	5.96×10^7
Aluminum	Conductor	3.50×10^7
Hard Rubber	Insulator	1.0×10^{-14}
Quartz	Insulator	1.30×10^{-18}
Silicon	SemiConductor	0.01 – 1000 [depending on doping]

Table 1.1: Electrical properties of various materials

Table 1.1 gives an overview of the conductivity of various materials.

Wires form the basis of our next idealization/abstraction. Although wire contain a complex lattice of various atomic structure we treat them in our circuit as perfect conductors of electricity which allow us to instant transfer an electric potential from one place in a circuit to another (i.e. lines of equipotential). In a circuit diagram we draw them as lines and in our conceptualization, we think of them as “electricity pipes” which current flows though without resistance.

Resistors and Resistivity

The conceptualization of current carrying wires as pipes leads to an oft-used and useful analogy in electronics: we can visualize the flow of charge as we would the flow of water through a pipe as sketched in figure 1.5. In this analogy voltage sources are replaced with hydraulic pumps and potential differences are pressure differences and current is fluid flow. The conductivity is given by the pump width.

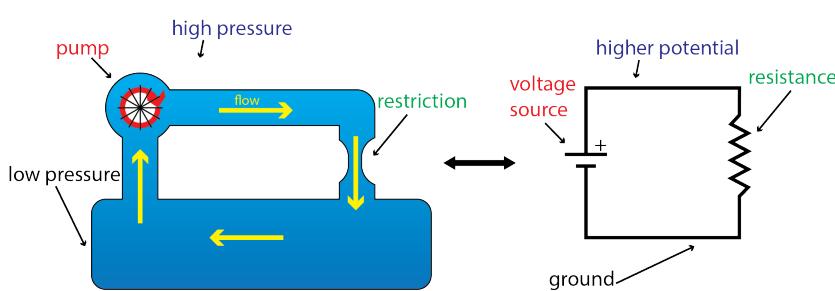


Figure 1.5: In the Hydraulic analogy, voltage sources are pumps, voltage is pressure, and resistance is pipe constriction.

As you may imagine from the above analogy a wide, short wire will have an easier time passing current than long thin one, which indeed turns out to be the case. The ease with which a given circuit element passes current for a given voltage is known as the resistance, defined as:

$$R \equiv \frac{V}{I} \quad (1.6)$$

It turns out that for a conductor, the resistance can be determined

from its geometry and conductivity, or as is most often used, its inverse – the resistivity:

$$\rho \equiv \sigma^{-1} \quad (1.7)$$

Specifically, for a wire with resistivity ρ , cross sectional area A and length L , the resistance is given by:

$$R = \rho \frac{L}{A} \quad (1.8)$$

Consistent with the water analogy the longer the wire, the higher the resistance, but this can be compensated by increasing its area (think of blowing through a long stir stick vs. a giant bubble tea straw – which is harder?).

For certain circuit elements the ratio in equation 1.6 is constant for all voltages. These devices are said to be “Ohmic” and obey *Ohm’s Law*.

$$V = IR \quad (1.9)$$

WARNING: many circuit devices are non-ohmic and do not satisfy Ohm’s law. In some texts, Ohmic just means a resistor, and non-Ohmic means anything else. To go further, **nothing** in nature is truly Ohmic since nothing is truly linear, but for Ohmic materials, the nonlinearity is so small that the point is moot. Whether or not a device is Ohmic can be determined by plotting voltage as a function of current by means of a so-called “IV curve”. An IV curve for a resistor and for a non-Ohmic device is shown in figure 1.6.

Resistors are constructed by taking a conductor with a given resistivity ρ and very carefully tuning the geometry to create a well defined resistance via equation 1.8. There are several design techniques: wire-wound resistors are made by taking a very thin wire and wrapping it around a coil until a desired length - and thus resistance is achieved. Thin film resistors take an opposite approach and tune the area of a fixed length film via the thickness. In either case the resistors are encased by an insulating material and placed in a compact package. Conducting leads allow the resistor to connect to other circuit elements. Figure 1.7 displays some of the existing technologies.

You may also notice colored rings on the resistors you use in the lab. This is the resistor color code that allows you to determine the resistance by cross-referencing with a look-up table. Such a table is included in the manual of Lab 1. Some gurus may take pride in memorizing the resistor color code and can tell you that you are holding a $12\text{ k}\Omega$ resistor just by looking at it.

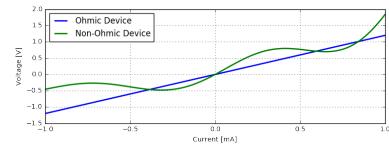


Figure 1.6: Many devices are non-ohmic. The ratio of voltage to current is constant for resistors (blue) which obey Ohm’s law. Other materials are non-Ohmic and have a non-constant slope (green)

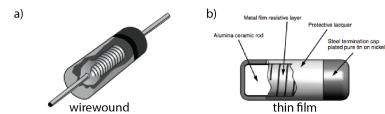


Figure 1.7: Sketch of a wirewound (a) and thin-film (b) resistor. Image from Vishay application note 28771

There are also variable resistors known as potentiometers which you will become familiar with in the lab. These work by having a moving conducting terminal which can slide along the resistor, continuously changing the length and therefore via eq. 1.8, the resistance.

Resistance of Non-Ohmic Devices

NOTE THE distinction between equations: 1.6 and 1.9. The latter implies that there is a linear relationship between voltage and current, and the ratio is the resistance. Equivalently, when plotted on an IV curve, the slope of the plot is the resistance.

This leads to two generalizations of resistance as either the ratio or the slope:

$$R_s = \frac{V}{I} \quad (1.10a)$$

$$R_d = \frac{dV}{dI} \quad (1.10b)$$

The quantity R_s is known as the “static resistance” and R_d is the differential resistance. Note that unlike static resistance which is necessarily positive, the a device can have negative differential resistance, meaning that R_s decreases with increasing current. The regions $-0.7 \text{ mA} < I < -0.3 \text{ mA}$ and $0.4 \text{ mA} < I < 0.7 \text{ mA}$ in figure 1.6 display this.

One common example of negative differential resistance is the fluorescent light bulbs which are installed in most office buildings. As more current flows, the bulb becomes more conductive. To circumvent a runaway process in which more and more current is drawn until a catastrophic failure (i.e. explosion) occurs, fluorescent lights are powered by “ballasts” that switch the current at high frequencies. In lab 10, you will construct an optical sensor to measure this switching frequency.

Electrical Power and Joule Heating

Ohms law tells us that when current flows through a resistor there is a drop in voltage and therefore a drop in the energy of each charge in the current. Given that energy is conserved, where does this energy go? It turns out that on the microscopic scale, the electrons comprising the current undergo inelastic collisions with the lattice of the material. It is just the likelihood of these elastic collisions which determine the conductivity/resistivity of the material.

Recall that in an inelastic collision, the particles lose kinetic energy and it this is just the case here. The electrons are accelerated by being in an electric potential until they collide with an ion in the lattice and bounce off, with less kinetic energy than they had before. Since the lattice ions are fixed, all of their motion goes into vibrations and we know this random atomic-lattice vibration as heat. This effect is known as *Joule Heating*.

As the electrons are dumping a given amount of energy per unit time due to the current, this heating is a power having units of Watts ($1\text{W} = 1\text{J/s}$). The general expression for the heating due to a current I across a potential difference V is remarkably simple, and is given by:

$$P = IV \quad (1.11)$$

For Ohmic materials, we can use Ohm's law to re-write this solely in terms of voltage and resistance:

$$P = I^2R = \frac{V^2}{R} \quad (1.12)$$

This is actually how incandescent light bulbs work. They are formed by a thin wire having a non-ohmic resistance⁴ and the Joule effect causes them to heat up until they glow white-hot. Older light bulbs are thus simply heaters that get so hot they happen to glow. They are also remarkably inefficient – only about 2% of their power is converted into visible light. A modern white-light LED on the other hand can reach nearly 50%.

⁴ The reason that the wire here is non-ohmic is that it heats up considerably which leads to more collisions and thus higher resistance

EXAMPLE 1.3

The resistance of a 60W light bulb

A 60W light bulb means that at wall-voltage (120V) the filament can safely absorb 60W of heat. What is the current of the light when operating at 60W? What is the static resistance?

Solution

From equation 1.11, we see that $I = P/V = 60\text{W}/120\text{V} = 0.5\text{A}$. Thus we see that a current of 500 mA is drawn. The (static) resistance is then

$$R_s = V/I = 120\text{V}/0.5\text{A} = 240\Omega$$

Connecting resistors

A real circuit does not typically contain a single battery pushing current through a single resistor. There is a network of resistors, and other components which we will learn about shortly. When

resistors are connected together they simply form a new resistor of a different resistance. Since resistors are two-terminal devices, it turns out that there are only two basic ways that a pair of resistors can be connected:

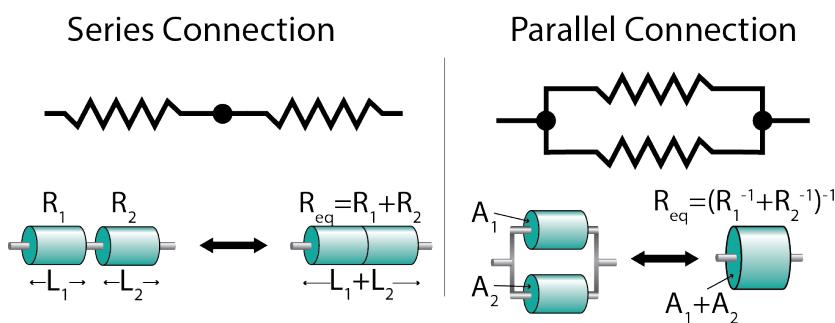


Figure 1.8: Sketch of Series and parallel connections

Series connection

In a series connection the resistors are placed end to end and all of the current is forced to flow through both resistors. The voltage drop is split between the two resistors. Referring to figure 1.8, we see that this is equivalent to increasing the length of the resistor and thus the resistance increases. To understand this more quantitatively, consider two resistors of equal area A and lengths L_1 and L_2 such that the resistances are R_1 and R_2 given equation 1.8. Connecting them in parallel then leads to a new resistor with length $L = L_1 + L_2$ with resistance $R = \rho \frac{L}{A} = \rho \frac{L_1}{A} + \rho \frac{L_2}{A} = R_1 + R_2$. This is true in general:

$$R_{\text{series}} = R_1 + R_2 \quad (1.13)$$

Parallel connection

In a parallel connection, the current is split between two resistors but the voltage drop is the same across both since they are connected to a common node. From the figure we see that two resistors in parallel are equivalent to a single resistor with greater area. The resistance of a series connection is thus less than that of its constituent resistors.

To get more quantitative again, consider two resistors with equal length L and resistivity ρ , but different areas A_1 and A_2 , yielding resistances R_1 and R_2 . The resistance of the parallel connection is given by $R = \rho \frac{L}{A} = \rho \frac{L}{A_1 + A_2}$. Therefore we have: $R^{-1} = \frac{A_1 + A_2}{\rho L} = \frac{A_1}{\rho L} + \frac{A_2}{\rho L} = R_1^{-1} + R_2^{-1}$. We thus arrive at the equivalent resistance of a

parallel resistance:

$$R_{\text{parallel}} = \left(R_1^{-1} + R_2^{-1} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2} \quad (1.14)$$

An Important Approximation: In many cases in practice, a series or parallel combination is completely dominated by one of the two resistors. Consider two resistors: $R_1 = 10 \text{ k}\Omega$ and $R_2 = 50 \Omega$. The parallel combination of the two gives $R_{\text{series}} = 10 \text{ k}\Omega + 50 \Omega = 10.05 \text{ k}\Omega \approx 10 \text{ k}\Omega$. On the other hand, the parallel connection gives $R_{\text{parallel}} = \frac{50\Omega \times 10^4\Omega}{10050\Omega} = 49.751\dots \approx 50\Omega$.

Thus if $R_1 \gg R_2$, the series combination gives $R = R_1 + \epsilon$ and the parallel combination gives $R = R_2 - \epsilon$ where $\epsilon/R \ll 1$.

More complicated combinations of resistors can always be reduced to an equivalent resistance. An example is given in figure 1.9. First, we see that the two $1\text{k}\Omega$ resistors in the top are just a series combination, equivalent to a single $2\text{k}\Omega$ resistor. This gives a parallel combination of two $2\text{k}\Omega$ resistors which is equivalent to a single $1\text{k}\Omega$ resistor. Finally, we are left with a series connection of 2 $1\text{k}\Omega$ resistors, so that the entire circuit is equivalent to a single $1\text{k}\Omega$ resistor.

⁵ “In the shop”, you rarely take the time to say “kilo-ohm” but say “kay” instead. Lazy, I know, but that’s how it is.

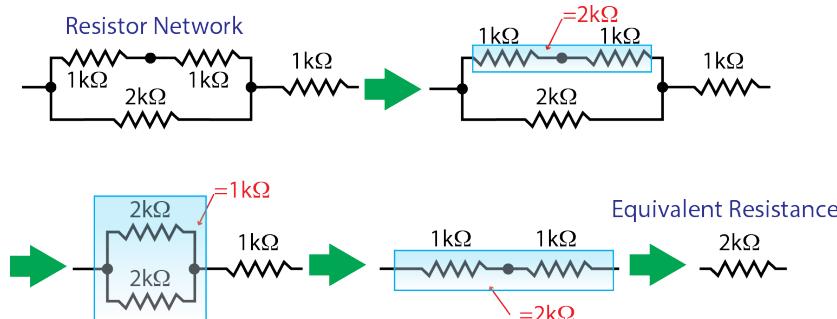


Figure 1.9: Example resistor network reduction.

Circuit Analysis Fundamentals

Now that we have an understanding of the fundamental components that make up a circuit, we can start designing and analyzing electronic circuits. The simplest circuits we'll look at are formed by connecting voltage sources and resistors with wires to form closed loops. This results in current flowing through resistors, and thus, according to equation 1.12, power is delivered to various elements in the circuits. So what do we mean when we say "analyze a circuit"? We "solve" a circuit by determining the voltage dropped across, current running through, and power dissipated within, any two points in the circuit. The following sections go through the basic techniques.

Elementary Circuit Analysis: An example

We can now use Ohm's law, along with the equations for parallel and series resistors to completely analyze a circuit. Not all circuits can be analyzed this way and for those, we will need a new method known as Kirchhoff's rules.


Consider the circuit in figure 1.10. Our goal will be to slowly fill in all the voltage drops and currents in this circuit and know all that there is to know about the circuit.

EXAMPLE 1.4 Analysis of circuit in figure 1.10

We can take a forward-backward sweep approach. What I mean is that we first reduce the resistors in the circuit so that we are left with the ultra simple circuit in figure 1.10c. This gives us the current supplied by the battery. Knowing the current we can use Ohms law to find voltage drops across the series resistances, which let's us determine the current through individual parallel combinations. Don't worry – it's easier done than said:

Step I Reduce the parallel combination ($a \rightarrow b$). From the rules for parallel resistors, we see that these two $2\text{ k}\Omega$ resistors are equivalent to a single resistor with

Figure 1.10: Elementary circuit analysis

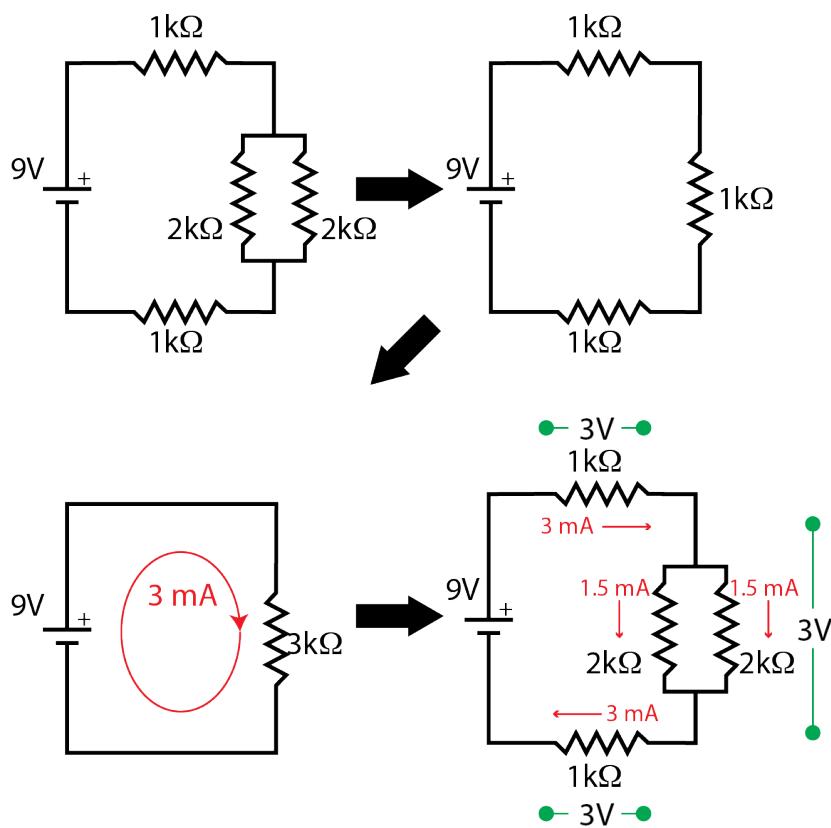

EXAMPLE 1.4

$$R = ((2 \text{ k}\Omega)^{-1} + (2 \text{ k}\Omega)^{-1})^{-1} = 1 \text{ k}\Omega.$$

Step II Reduce the remaining parallel resistors into a single battery, single resistor circuit ($b \rightarrow c$). We have 3 $1 \text{ k}\Omega$ resistors in series, equivalent to a single $3 \text{ k}\Omega$ resistor. When connected to a 9 V battery, this gives a current of 3 mA.

Step III Work backwards and determine everything about the circuit ($c \rightarrow d$). We see the voltage drop across the parallel resistors and the two $1 \text{ k}\Omega$ resistors is $V = IR = 3 \text{ mA} \times 1 \text{ k}\Omega = 3 \text{ V}$. The current through the $2 \text{ k}\Omega$ resistors is $I = V/R = 1.5 \text{ mA}$ and we know all there is to know about this circuit.

Measuring DC quantities: The Digital Multimeter

The Digital Multimeter (DMM)

A voltmeter is a device that measures the potential difference across two points on a circuit when placed in parallel across the two points. Similarly, an ammeter measures current through a wire by inserting itself in series with the wire. An ohmmeter measures the value of a resistor.

Thankfully there is a very common device known as a digital multimeter (DMM) which does all three - and more. The “digital” part of it means that the continuous (or analog) quantities measured are converted into digital format via an aptly named *analog to digital converter* or ADC which we will study later in the course. You will use make heavy use of a DMM in every one of your labs. The procedure for the 3 basic measurement are described as follows:

Voltage

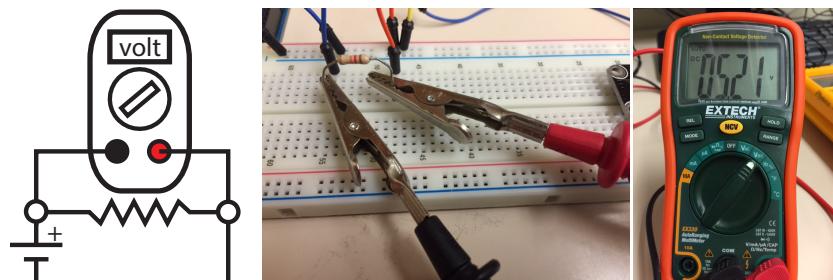


Figure 1.11: Measuring Voltage

When measuring **voltage** between two points on a circuit, first ensure your probe ends are connected to the correct inputs of the Digital Multimeter (DMM) for measuring a DC voltage, and that the voltage setting is selected. Probe tips can then be placed in parallel across the circuit (Fig. 1.11). The circuit does not need to be modified for this measurement, making voltage measurements relatively straightforward. From voltage measurements and known resistances, the current through the circuit can be inferred from Ohm’s law, however the DMM can be configured to measure resistance and current directly.

Current

In contrast to voltage measurements, **current** measurements are performed in series along the circuit. First ensure your probe ends are connected to the correct DMM inputs for measuring current. When

you connect your probe tips, it is essential that the DMM is wired in series with the current being measured. If it is properly wired in series, the current will be forced to flow through the DMM (Fig. 1.12) and a measurement can be made.

Warning: The DMM measures current by measuring the voltage dropped across a calibrated resistor of very small resistance. Measuring current in parallel will draw high current through the DMM and blow a fuse. **Do not measure current in parallel!**

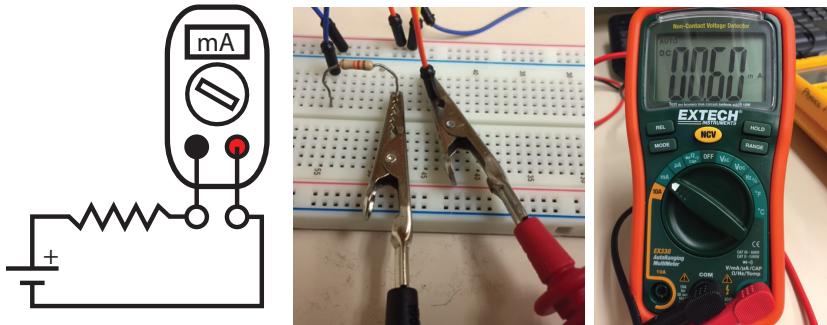


Figure 1.12: Measuring Current

Resistance

When measuring **resistance**, it is important to isolate the resistor in question (i.e. remove it from the circuit) as shown in Fig. 1.13. If left connected, the DMM measures the series connection of the resistor and the rest of the circuit. Ensure your probe ends are connected to the correct DMM inputs for measuring resistance.

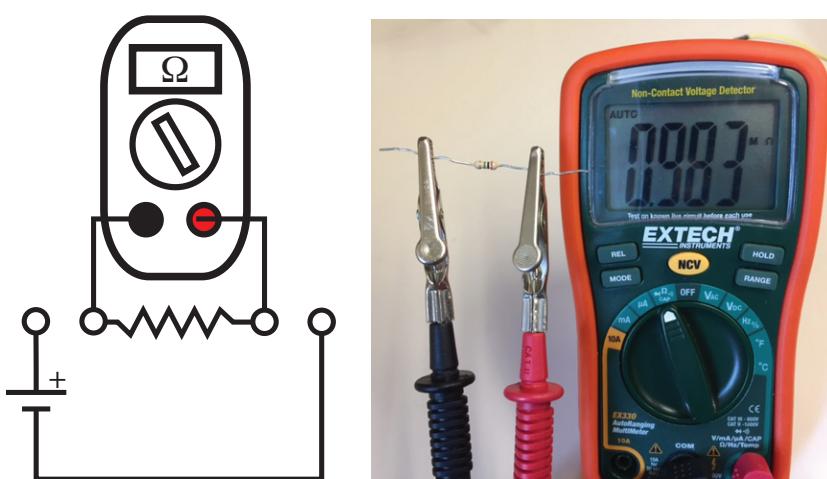


Figure 1.13: Measuring Resistance

Amplifiers

Active vs. Passive Circuits

We now move into the regime of so-called *active electronics*. Everything studied so far – resistors and capacitors, to voltage dividers and filters, to diode rectifiers has fallen under the realm of passive electronics. Active electronic devices, in addition to standard inputs and outputs, require additional power supplies in order to function. There are great benefits to this, as we shall see: active components can output more power than at their input, and can eliminate annoying effects such as voltage loading due to input and output impedance. The first active device we'll study is the amplifier.

The Ideal Voltage Amplifier

The idea of the basic amplifier is simple: take the input x_{in} and produce an output which is some number G times the output.

$$x_{\text{out}} = Gx_{\text{in}} \quad (1.15)$$

... where G is known as the gain.

There is the question of what input x_{in} is being amplified. In our course, normally x_{in} will be a voltage and so we will have a voltage amplifier. In this case the gain is often expressed in decibels as:

$$G_{\text{dB}} = 20 \log \frac{v_{\text{out}}}{v_{\text{in}}} \quad (1.16)$$

We will occasionally deal with power amplifiers whose input and output is a power. For these amplifiers, the gain is also in dB but with a 10 instead of a 20 multiplier⁶:

$$G_{\text{dB}} = 10 \log \frac{P_{\text{out}}}{P_{\text{in}}} \quad (1.17)$$

For now though, we will restrict ourselves to voltage amplifiers.

Diagrammed in figure 1.14. The output is described by equation 1.15.

⁶ Recall that for a fixed load resistance, $P = v^2/R \propto v^2$. Thus $10 \log [P_{\text{out}}/P_{\text{in}}] = 10 \log [(v_{\text{out}}/v_{\text{in}})^2] = 20 \log [v_{\text{out}}/v_{\text{in}}]$, thus yielding consistent definitions of gain

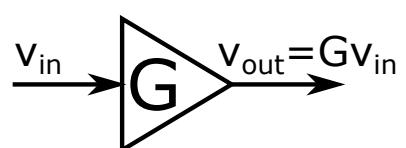


Figure 1.14: The simplest of amplifiers: the output is the input multiplied by a constant gain G .

Reality Check: Amplifiers in Real Life

There are several limitations to the ideal amplifier that come into effect in practice. For example the amplifier will have to draw at least a small current from the source in order to operate. As we've learned, this is equivalent to a finite *input impedance* R_{in} . The amplifier will also have a limit to how much current it can output due to its internal resistances. This leads to a finite *output impedance* R_{out} . There are also limits to how fast the amplifier can respond to a changing input signal. This leads to a finite *gain bandwidth*, or in general, a frequency dependent gain $G(\omega)$. We will examine each of these effects presently.

Effects of Finite Input Impedance

We can model the non-ideal amplifier as an ideal amplifier inside a black box, precisely as we did with ideal vs real voltage sources. Inside the black-box, the input impedance is models as an internal resistance R_{in} to ground placed before the ideal amplifier. This forms a voltage divider with the input impedance from the rest of the circuit so that there is some voltage drop. The ideal amplifier thus sees a different voltage than v_{in} , which we denote v'_{in} . The output of the real amplifier is thus less than we would expect: $v_{out} = Gv'_{in} < Gv_{in}$

The true output, given the input impedance can be calculated given the output impedance of whatever follows. For example, with a 100Ω input impedance amplifier with $G = 10$,

Effects of Finite Output Impedance

The operation of our ideal amplifier can be seen as a two part process: first it senses the voltage at its input (with the effect of finite input impedance causing some loading error), and second, it acts as a new voltage source, producing a voltage $v_{out}Gc_{in}$. As with any *real* source, it will be equivalent to an ideal source, in series with an output impedance R_{out} . This finite output impedance leads to a maximum short-circuit current of v_{out}/R_{out} and will lead to all of the loading issues discussed in chapter XXX. Figure 1.16 shows our improved model of how a real amplifier behaves.

Design Example: Consider a real amplifier with $R_{in} = 10 \text{ k}\Omega$, $R_F = 100 \Omega$, and $G = 25$. We use it to amplify a 10 mV signal from a photo-detector having $R_{out,PD} = 1250 \Omega$ and send it to a (lousy) voltmeter with $R_{in,LVM} = 500 \Omega$ (see figure 1.17). What is the voltage measured (a) assuming an ideal $G = 25$ amplifier, and (b) with our real amplifier?

Answer: For part (a) the answer is simply $v_{meas} = 25 \times 10 \text{ mV} =$

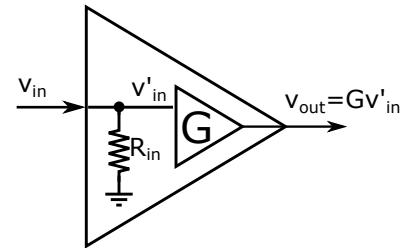


Figure 1.15: We model the finite input impedance of the amplifier as a internal resistor R_{in} to ground before an ideal amplifier all in a black box.

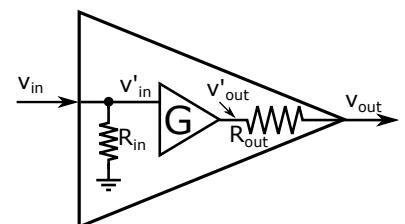


Figure 1.16: A better model of a real amplifier has an input resistance to ground in parallel with the input and an output resistance in series with its output.

250 mV. For our real amplifier, we must consider the input and output stage. The input now forms a voltage divider with R_{in} (figure 1.17b) so that the inner ideal amplifier sees:

$$v'_{in} = \frac{R_{in}}{R_{out,PD} + R_{in}} = \frac{10 \text{ k}\Omega}{11.25 \text{ k}\Omega} \times 10 \text{ mV} \approx 8.9 \text{ mV}$$

In our model, this is then amplified by the ideal internal amplifier producing

$$v'_{out} = 8.9 \text{ mV} \times 25 \approx 222 \text{ mV}$$

Finally, this is then sent to our lousy voltmeter, through its internal output resistance, forming another voltage divider (figure 1.17c) to yield the final voltage:

$$v_{out} = \frac{R_{in,LVM}}{R_{out} + R_{in,LVM}} v'_{out} = \frac{500 \Omega}{600 \Omega} \times 222 \text{ mV} \approx 185 \text{ mV}$$

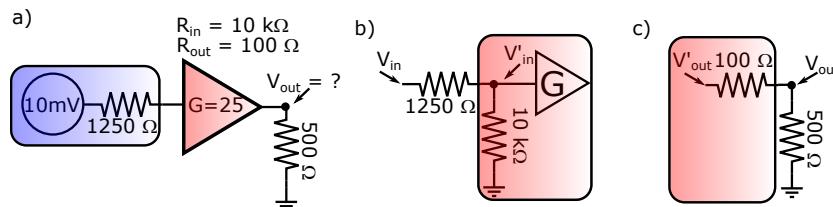


Figure 1.17: Example Problem.

We thus see that the effect of finite input and output impedance is to lessen the effective gain of the real amplifier. Even if we used an ideal voltmeter with infinite input impedance, we'd still see 222 mV < 250 mV. Equivalently, we could try to build an amplifier with $R_{out} \rightarrow 0 \Omega$ and again we'd see 222 mV, regardless of the impedance of the voltmeter. To get the full 250 mV however, we'd need to also have $R_{in} \rightarrow \infty$, so that $v'_{in} = v_{in} = 25 \text{ mV}$.

From this we can infer the ideal characteristics of a real amplifier: we want the input impedance as high as possible while having output impedance as low as possible. This can be accomplished using solid state transistors, discussed later in the course.

Effects of Noise: Noise Factor and SNR

The ideal amplifier will amplify the voltage present at its input, regardless of whether we consider that voltage to be useful signal or to be noise. This can lead to fundamental issues in isolating very weak signals since eventually, we will just be scaling up Johnson, Shot, or technical noise.

For example, if you have a 10 nV signal atop 25 nV of Johnson noise, you can send your signal to a 120 dB amplifier to get 100 mV

of signal, but it will still be lost in the Johnson noise, which is now at 250 mV. We amplified the signal level, but have not improved the signal level as compared to the noise. This ratio of signal vs noise has, in a spark of linguistic creativity, been dubbed the “signal to noise ratio” or SNR. since the voltage of the noise is usually stochastic⁷, usually the signal to noise ratio is usually specified in terms of power, rather than voltage⁸ (i.e. v_{RMS}^2/R)

$$\text{SNR} \equiv \frac{P_{\text{sig}}}{P_{\text{noise}}} = 10 \log_{10} \left[\frac{P_{\text{sig}}}{P_{\text{noise}}} \right] \text{dB} \quad (1.18)$$

So an amplifier on its own will not help you discern signals dominated by noise and the SNR must be improved though separate means. If your signal exists within a given range of frequencies but your noise exists at all frequencies, a filter can be applied to the input of the amplifier to greatly improve the SNR. If the signal and noise coexist at the same range of frequencies, you have to be more clever. For example, a common source of noise is thermal motion of electrons through a load resistance. To improve the SNR, circuits are often cooled to -40 °C or even as low as several Kelvin, when extremely faint signals are being detected.

To make matters worse, the amplifier often adds its own noise to the system - that is the SNR of the output is typically even higher than that of the input! This is quantified by the so-called noise figure:

$$\text{NF} \equiv \frac{\text{SNR}_{\text{out}}}{\text{SNR}_{\text{in}}} = 10 \log_{10} \left[\frac{\text{SNR}_{\text{out}}}{\text{SNR}_{\text{in}}} \right] \quad (1.19)$$

Good amplifiers will have NF 2 dB or less.

Effects of Finite Frequency Response

Since every circuit element has some finite capacitance and inductance, we can replace the internal input and output resistances with an input impedance Z_{in} and output impedance Z_{out} . The net effect of this is to produce a frequency dependent gain $G(\omega)$. This can be modeled as internal frequency filter that is applied to the input or output. This bug can be re-branded as a feature as an amplifier may actually filter out high frequency noise present in the signal, as discussed in the previous section.

Differential Amplifiers

Often in physics, it is a small deviation from a fixed value that is of interest rather than the absolute value itself. For example, a beam of light may pick up a small oscillation in intensity as compared to a reference beam when passed through a sample. In this case, a

⁷ A high-brow term, effectively meaning “random”

⁸ ...wait, what R should we use here? Well power is energy per unit time and that energy has to be delivered to something. That something is the load resistance, so that a given voltage noise will deliver more power to a 100 Ω than a 100 kΩ resistor

differential amplifier may be used. As diagrammed in figure 1.18, a differential amplifier has two inputs and a single output corresponding to the difference between the signals. This is operation can be seen as first inverting one input and then adding it to the other. The input which is inverted V_- is fitting called the “inverting input”, while the normal input is verbosely titled the “non-inverting input”, V_+ . The multiplication factor is known as the “differential gain” G_{diff} and is defined through the relation

$$v_{\text{out}} = G_{\text{diff}} (v_+ - v_-). \quad (1.20)$$

Example: A differential amplifier with $G_{\text{diff}} = 40$ dB has, at its inputs: $v_+ = 3.7$ mV and $v_- = 4.2$ mV. What is the output voltage?

Solution: The gain of 40 dB implies that $20 \log_{10} \frac{v_{\text{out}}}{v_+ - v_-} = 40$, so that $v_{\text{out}} = 100 (v_+ - v_-)$. Since, $(v_+ - v_-) = (3.7 - 4.2)$ mV = -0.5 mV, we will find $v_{\text{out}} = -500$ mV.

Common Mode Gain

From equation 1.20, we expect that if $v_+ = v_-$, we will have $v_{\text{out}} = 0$ regardless of the value of v_+ and v_- . In practice however, this is not the case. This can be due, for example, to differences in the input impedances of the individual inputs so that internally, $v'_- \neq v'_+$ even though $v_- = v_+$ (see the previous section). To quantify this, we define the *common-mode voltage* as the average of the inverting vs. non-inverting input voltages:

$$v_{\text{com}} \equiv \frac{v_+ + v_-}{2} \quad (1.21)$$

The amount of signal that gets through defines the *common-mode gain*

$$v_{\text{out}} = G_{\text{com}} \frac{v_+ + v_-}{2} \quad (1.22)$$

An ideal differential amplifier would have $G_{\text{com}} = 0$ or $-\infty$ dB. The true output of the *real* differential amplifier is thus:

$$v_{\text{out}} = G_{\text{diff}} (v_+ - v_-) + G_{\text{com}} \frac{v_+ + v_-}{2}. \quad (1.23)$$

Common Mode Rejection Ratio

The “goodness” of a differential amplifier is how much it behaves like one! Mathematically we can quantify this by saying that for a good differential amp, $G_{\text{com}} \ll G_{\text{diff}}$. THis is represented by the so-called “common-mode rejection ratio” or CMRR. The CMRR is usually stated in decibels and is given by:

$$\text{CMRR} \equiv 20 \log_{10} \left[\frac{G_{\text{diff}}}{G_{\text{com}}} \right] \quad (1.24)$$

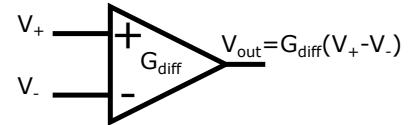


Figure 1.18: A Differential Amplifier.

Decent differential amplifiers have CMRR^s of at least 70 dB but some applications require 120 dB or higher.

Feedback and Op Amps

By far and wide, the amplifier that you will see the most of in the labs is a very high gain, differential amplifier known as an “operational amplifier”, or *Op Amp*. Op-amps form the basis of a very wide range of applications: adding and subtracting voltages, frequency filters, low-noise single-input amplifiers, circuit protection, oscillators/function generators, and analog to digital converters, (to name a few). The typical differential gain of an op-amp is insanely high - 1,000,000 or higher. The gain is so high in fact that it renders opamps useless when used as standard differential op-amps. The utility of an op-amp comes in by employing the crucial concept of negative feedback, which we will explore presently.

Negative Feedback

Feedback refers to a configuration in which the output of a system is connected back into its input (i.e. “fed back”). Feedback systems are everywhere in nature: in the human body the amount of insulin in the bloodstream is sensed and fed back into beta cells in the pancreas which determine the amount of insulin to be secreted. In climatology, a mechanism for ice ages is thought to be that colder weather creates more snow and thus more light is reflected back into space, creating more snow, etc. Of course, feedback systems can be engineered by us humans as well. The formal theory of feedback is a part of the field known as control theory.

A simple feedback system is shown in figure 1.19a.

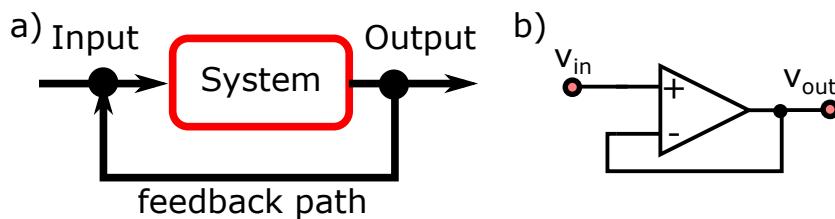


Figure 1.19: a) The simplest feedback system. b) Opamp in negative feedback configuration. If the output was wired to the non-inverting input, it would be “positive feedback”.

Op Amps in Negative Feedback: The Golden Rules

Let's observe the operating characteristics of an ideal opamp, operating in a simple negative feedback configuration as diagrammed in figure 1.19b. We can look at both in terms of an abstract feedback system and also try to get a picture of what's going on "under the hood". Let's start with the former: We don't know what the output actually is, but from the definition of a differential amplifier (equation 1.20), and from the fact that the output is wired to the inverting input (hence negative feedback) we see that $v_+ = v_{\text{in}}$ and $v_- = \text{out}$. Thus:

$$v_{\text{out}} \equiv G(v_+ - v_-) = Gv_{\text{in}} - Gv_{\text{out}}$$

... so that

$$v_{\text{out}} = \left(\frac{G}{G-1} \right) v_{\text{in}} \quad (1.25)$$

In the limit of an ideal opamp, $G \rightarrow \infty$ so that this becomes $v_{\text{out}} = v_{\text{in}}$. Congratulations, we've just made the world's most useless circuit. Or have we? In fact, although I chose this as a simple way to understand opamps, this circuit, known as a "buffer op-amp" is indeed very useful and is found everywhere. Why? Because of the other property of the opamp - the insanely high input impedance. This means that the non-inverting opamp "sniffs-out" the input voltage while drawing negligible current, reproducing the voltage at the output and providing whatever current is called for. But where does this current come from if not the input? It turns out that we forgot to draw all of the opamp's terminals on our sketch - op-amps are active components and thus need power. Whatever power is needed for the output essentially comes from the power terminals and our buffer opamp thus separates whatever is on the input side of the circuit from the components on the output. We can drive large amounts of current without disturbing the sensor, voltage divider, or whatever is going into the circuit. No loading error, near zero output impedance. The buffer opamp creates a signal and converts it into a near-ideal source.

The above example illustrates the most important features of opamps in negative feedback. They are so useful in understanding how opamps behave, that they have been dubbed "The Golden Rules of OpAmps":

Golden Rule I: The opamp draws no current at its inputs: $i_+ = i_- = 0$.

Golden Rule II: In negative feedback, the opamp's output adjusts itself so that its inputs are equal $v_+ = v_-$.

The first rule is merely a restatement that opamps have very large

input impedance. The second rule is a property of negative feedback, but is less obvious than the first. To understand why it must be so, let's reanalyze the previous example in a more empirical manner. Consider again the circuit in figure 1.19b. Suppose we have just switched the circuit on and the output is some random value (I don't know ... -1.234 V say) and the input is at 3 V. The input sees a voltage difference of 4.234 V and immediately starts trying to put out an enormous, positive voltage (although it can't switch instantaneously, since there's always some capacitance inductance and resistance in the circuit.) Thus a split second later, the output difference has been reduced, say to +2V. Now the output difference is 1 V and again the output tries to become more positive (but less than before.) After a short time the output reaches +3 V and the output no longer tries to swing to a more positive value. Suppose that it overshoots 3 V (due to its small parasitic inductance) so that the voltage is now at 3.1 V. The difference voltage is now -0.1 V and the output now starts becoming negative. We see the action of negative feedback on the system – when the output is lower than the input it quickly becomes larger and when it is higher, it quickly becomes lower. The only stable configuration is where the output equals the input. This is why **GR II** works.

Of course, we can do much more with opamps than to create a voltage buffer. There are, quite literally, shelves in libraries filled with entire books on opamps. We'll go through the more common opamp applications in the following sections. We can use the golden rules of opamps throughout to analyze the functionality of these circuits.

Inverting Opamps

The next simplest opamp to analyze is the inverting opamp, seen in figure 1.21a. Here the gain is a negative number so that a positive input produced a negative output and vice versa.

To understand the functionality of this opamp, we apply the golden rules. First, since the non-inverting output is shorted to ground **GR II** tells us that the noninverting terminal is also clamped to ground. In this situation, the node at the inverting terminal is said to be a *virtual ground*. The current through the first resistor R_1 is thus:

$$i_{R_1} = \frac{v_+}{R_1} \quad (1.26)$$

Next, **GR I** tells us that no current runs into the v_+ terminal so that by Kirchhoff's rules, $i_{R_2} = i_{R_1} = v_+/R_1$. This allows us to determine the voltage drop across the second resistor R_2 (note now

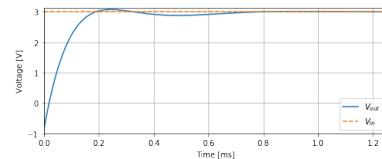


Figure 1.20: Feedback quickly settles the output value to whatever the input happens to be.

that the voltage goes from 0 to something lower):

$$0 - v_{\text{out}} = i_{R_2} R_2 = \frac{R_2}{R_1} v_+ \quad (1.27)$$

This gives us the output of the inverting opamp:

$$v_{\text{out}} = - \left(\frac{R_2}{R_1} \right) v_+ \quad (1.28)$$

The gain is negative and adjustable by adjusting R_1 or R_2 .

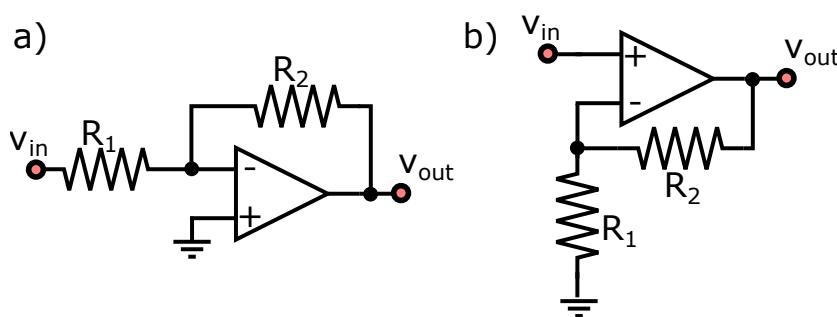


Figure 1.21: a) Inverting opamp with gain $G = -R_2/R_1$. b) Non-inverting opamp with gain $G = 1 + R_2/R_1$

Non-Inverting Opamps

The next opamp that we will analyze is the “non-inverting” opamp of figure 1.21b. Here we can use the second golden rule to note that the inverting terminal is held at whatever v_{in} is. In order to determine the output voltage, we note again that **GR I** tells us that no current runs into the v_- terminal and so that R_1 and R_2 form a voltage divider from v_{out} to ground with $v_- = v_{\text{in}}$ as the intermediate voltage:

$$v_{\text{in}} = \frac{R_1}{R_1 + R_2} v_{\text{out}} \quad (1.29)$$

Rearranging to solve for v_{out} , we find:

$$v_{\text{out}} = \left(1 + \frac{R_2}{R_1} \right) v_{\text{in}} \quad (1.30)$$

Although the noninverting output has the benefit of a positive gain, a limitation is that unlike its inverting counterpart, it can not have $|G| < 1$.

Differential Amplifiers

Although the ultra-high gain of an opamp makes it fairly useless as a direct differential amplifier, we can make a differential amplifier

circuit using an opamp. The use of feedback can ensure low output impedance, tunable differential gain, and high CMRR.

The opamp-based differential amplifier is shown in figure [zzz]. Pairs of matched resistors (R_1, R_2) are used for the feedback path. As usual, we can derive the output in terms of the golden rules: **GR I** tells us that the top and bottom paths form voltage dividers between $v_1 \rightarrow v_{\text{out}}$ and $v_2 \rightarrow \text{GND}$ respectively, ie.

$$\frac{v_- - v_{\text{out}}}{v_1 - v_{\text{out}}} = \frac{R_2}{R_1 + R_2}$$

$$\frac{v_+ - 0}{v_2 - 0} = \frac{R_2}{R_1 + R_2}$$

... rearranging, we find:

$$v_- = \frac{R_1 v_{\text{out}} + R_2 v_1}{R_1 + R_2} \quad (1.31)$$

$$v_+ = \frac{R_2}{R_1 + R_2} v_2 \quad (1.32)$$

From **GR II** we know that these inputs are equal. Equating them and multiplying both sides by $R_1 + R_2$, we find $R_2 v_2 = R_1 v_{\text{out}} + R_2 v_1$, or

$$v_{\text{out}} = \frac{R_2}{R_1} (v_2 - v_1) \quad (1.33)$$

We thus have a differential amplifier with adjustable gain (R_2/R_1). There are two issues with this design however. First, it requires perfectly matched resistors or else the output will not be directly proportional to the voltage difference. Next, small differences in the input stages of real opamps lead to imperfect cancellation of common mode signals. For this reason, some opamps provide extra “offset-null” pins which can be used to compensate for these differences. In the lab you will build your own differential opamp and do just this.

Differentiator and Integrator Opamps

We now consider the effect of general impedances in the construction of opamp feedback circuits. Fortunately, our generalized Ohm’s law analysis that we analyzed earlier allows us to quickly determine the gain of the circuit, which when using reactive components is generally frequency dependant.

Differentiator Circuit

Consider first, the circuit in figure 1.22a. **GR I** tells us that the current through the capacitor is equal to that of the resistor $i_C = i_R \equiv$

$(v_- - v_{\text{out}})/R$, while **GR II** tells us that v_- is a virtual ground ($v_- = 0$). Recalling the definition of a capacitor:

$$i_C = C \frac{dv_C}{dt} \quad (1.34)$$

we have, noting $v_C = v_{\text{in}}$:

$$v_{\text{out}} = -RC \frac{dv_{\text{in}}}{dt} \quad (1.35)$$

... i.e. the output is the derivative of the input voltage, scaled by a factor of $-RC$.

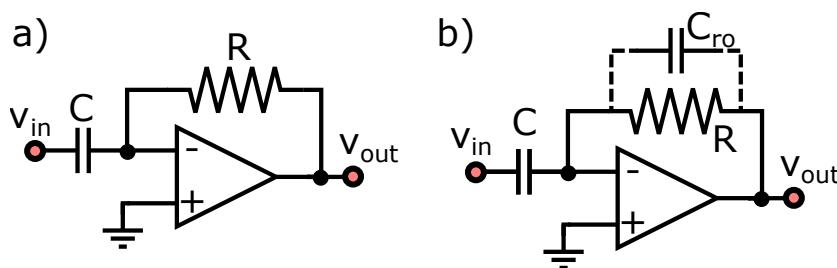


Figure 1.22: a) Differentiator opamp: $v_{\text{out}} = -RCv'_{\text{in}}(t)$. b) The addition of a “roll-off” capacitor fixes the differentiator’s susceptibility to high frequency noise.

A better Differentiator Circuit

A problem with derivatives is that very fast signals will produce enormous outputs. Even small amounts of noise can be greatly amplified, for a Fourier component at frequency ω , given by $v_\omega(t) = v_0 e^{j\omega t}$ has a derivative with magnitude:

$$\left| \frac{dv_\omega(t)}{dt} \right| = \omega |v_\omega(t)|$$

Thus a $1 \mu\text{V}$ signal at 10 MHz will have an amplitude of over 30 V ! A standard trick to overcome this is to put a small, roll-off capacitor C_{ro} in parallel with the feedback resistor (figure 1.22b). At lower frequencies ($\omega \ll 1/RC_{\text{ro}}$) the extra capacitor has very high resistance and the feedback current is completely dominated by the resistor ($Z_2 \approx R$). The situation is identical to the previous analysis. For very high frequencies however, the capacitance now has vanishing impedance and the current would rather ignore the resistor and take this path ($Z_2 \approx -j/\omega C_{\text{ro}}$) and the gain rolls off to zero at high frequencies.

Integrator Circuit

A slight modification to the differentiator circuit is shown in figure 1.23a. Here the non-inverting input is still held at a virtual ground

but the positions of the resistor and capacitor are swapped. Now, we have

$$i_C = -C \frac{dv_{\text{out}}}{dt} = \frac{v_{\text{in}}}{R}$$

Integrating this equation gives

$$v_{\text{out}}(t) = -\frac{1}{RC} \int_{t_0}^t v_{\text{in}}(t) dt = -\frac{1}{RC} \int v_{\text{in}} dt + k_0 \quad (1.36)$$

so that we have an output that is the integral of the input. The constant of integration is given by the value of the input at t_0 , i.e. $k_0 = -\frac{v_{\text{in}}(t_0)}{RC}$.

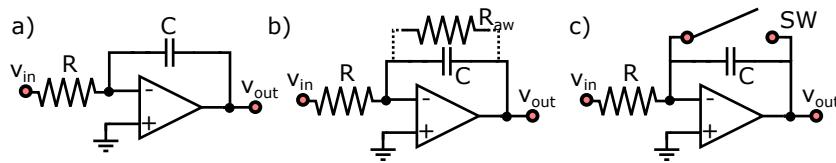


Figure 1.23: a) Integrator opamp: $v_{\text{out}} = -\frac{1}{RC} \int v_{\text{in}}(t) dt$. b) The addition of an “anti-windup” resistor prevents a DC bias from overwhelming the signal. c) Alternatively, a “reset switch” can reset the initial condition to 0 V.

A Better Integrator Circuit

Much like the differentiator, the integrator circuit experiences its own drawbacks. The primary is that of “wind-up”. Wind-up is merely a statement that the integral of a constant is a constantly increasing (or decreasing) signal. Suppose that your signal is 0 V to 1 V sine wave at frequency $\omega = 2\pi \times 5 \text{ Hz}$ and is input to an $R = 5 \text{ k}\Omega$, $C = 10 \mu\text{F}$ integrator. You might expect that the output will be:

$$v_{\text{out}} = -\frac{1}{RC} \int \sin(\omega t) dt = \frac{1000 \text{ s}^{-1}}{\omega} \cos(\omega t) \approx 0.637 \text{ V} \cos(2\pi \times 5 \text{ Hz})$$

but instead, will find strange behavior. Figure 1.24 displays the resultant output when an opamp with $\pm 3.3 \text{ V}$ supply rails are used. The output gradually drifts downward until eventually becoming a constant -3.3 V. What went wrong? Well our 0-1 V sine wave is really not a pure sine wave but a 0.5 V amplitude sine wave plus a 0.5 V constant offset. The output is then:

$$v_{\text{out}} = -\frac{1}{RC} \int 0.5 (\sin(\omega t) + 1) dt \approx 0.637 \text{ V} (\cos(\omega t) - t)$$

... i.e. a cosine wave with a constantly decreasing offset which eventually exceeds the supply rails. This is an example of windup. There are two basic ways of resolving the issue. One way is to use a feedback resistor in parallel with the capacitor (figure 1.23b), so that at

very low frequencies (and at DC) the near-infinite impedance of the capacitance is bypassed by the “anti-windup” resistor, capping the gain at $-R_{aw}/R$. A second way is to place a manual or automatically activated switch in place of R_{aw} (figure 1.23c) which shorts the gain to zero. This can be seen as setting the initial condition to zero.

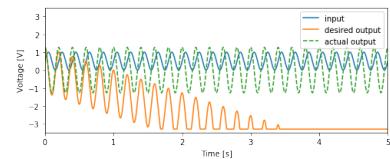


Figure 1.24: Windup error.